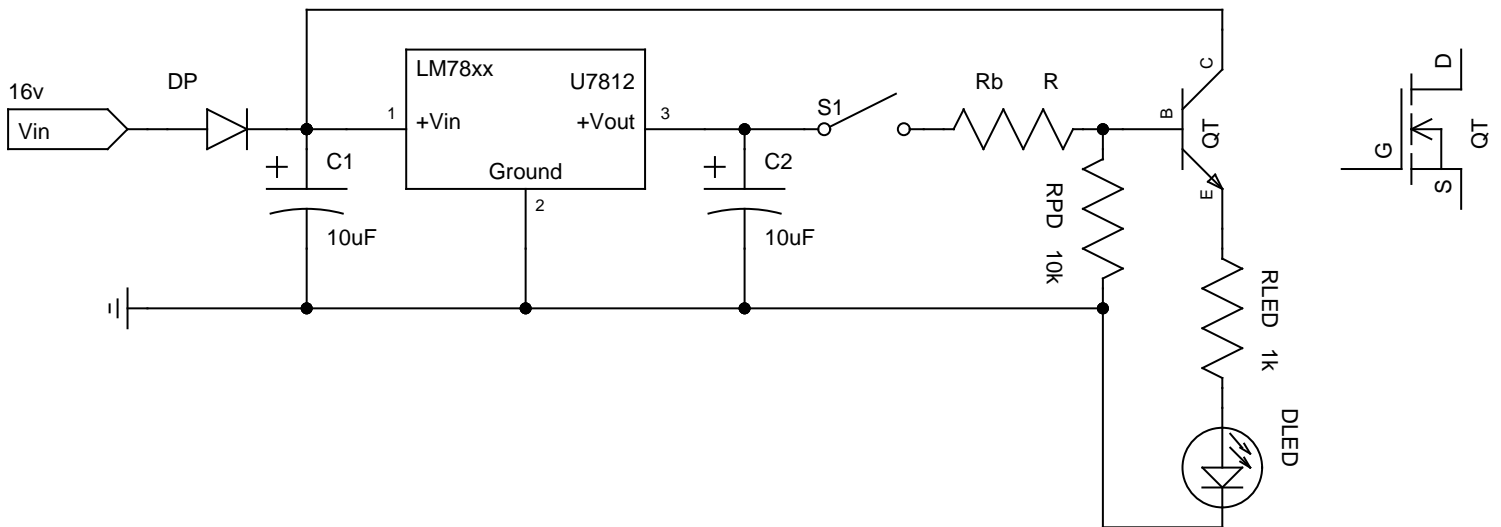


Simple Transistor Checker (N Type)



Plug in the transistor in question (NPN or N-MOSFET) where the transistor is shown.

With the switch open, the LED should not light up. With the switch closed, it should.

If the device under test responds in a different way, it is broken.