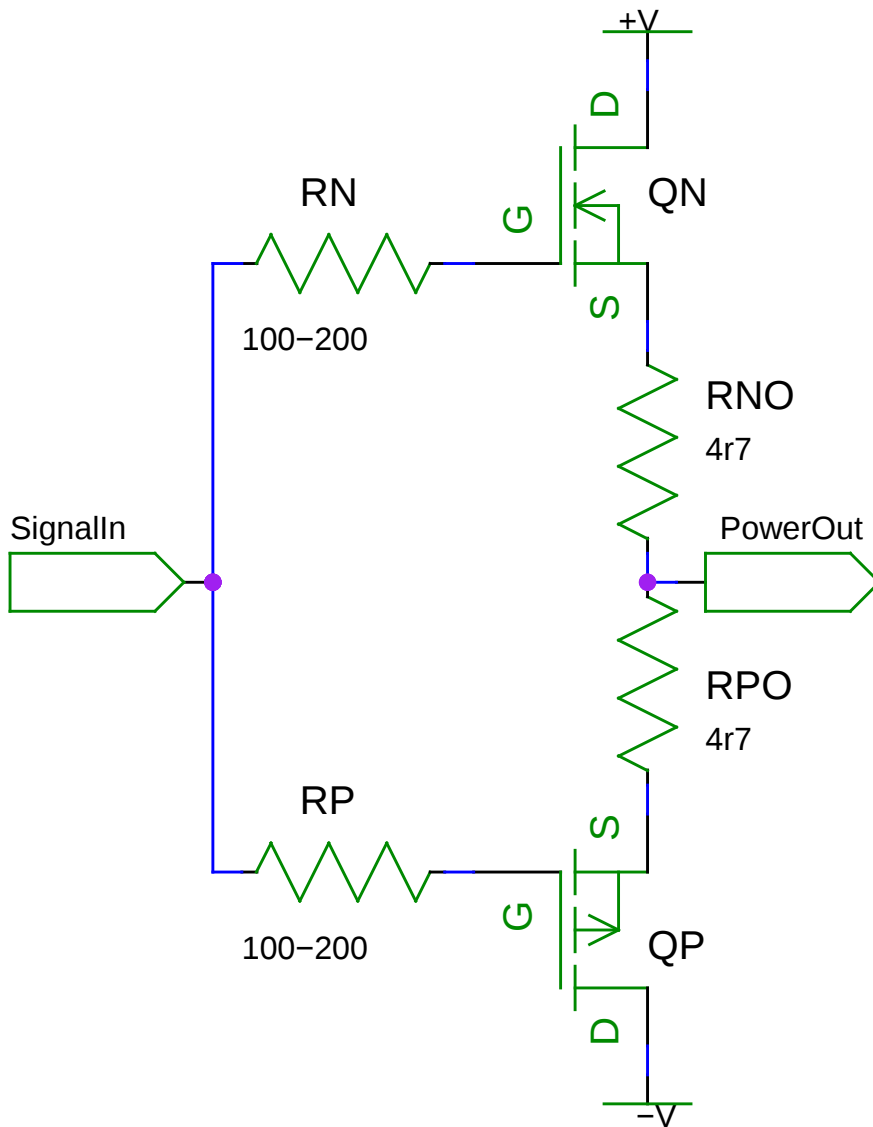


MOSFET Output Boosters

2011-02-27



MOSFET output boosters are nearly identical to BJT, so only part is shown.

The N-Channel replaces the NPN, and P-Channel the PNP.

The MOSFETs should be enhanced mode.

Linear MOSFETs are harder to find. Switching ones should not be used.

Look for key words: power, planar, lateral, non-vertical, non-switching.